


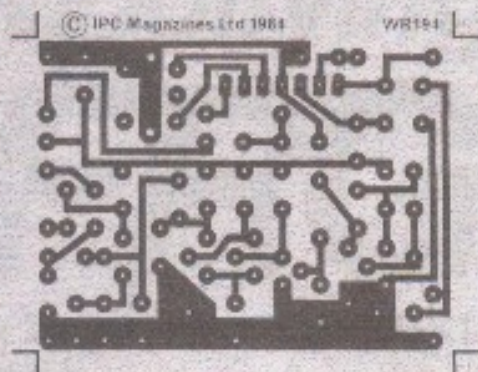


Fig. 3.2: The p.c.b. layout for the f.m. adaptor and all-mode squelch unit. Note the prefix letter Y has been omitted for clarity

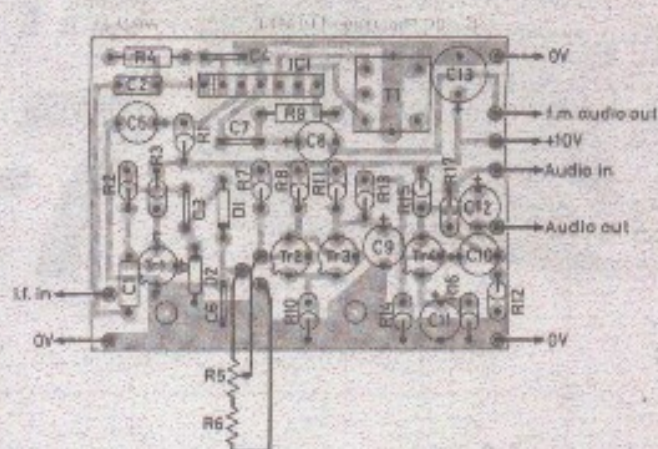

WRM230

★ components

Resistors

$\frac{1}{4}$ W 5% Carbon film

100 Ω	1	YR1
390 Ω	1	YR10
1k Ω	4	YR3, 6, 12, 16
2.2k Ω	2	YR4, 9
5.6k Ω	1	YR15
10k Ω	3	YR8, 11, 17
15k Ω	1	YR14
22 Ω	1	YR7
100k Ω	2	YR2, 13

Logarithmic potentiometer (reverse)

10k Ω	1	YR5
--------------	---	-----

Capacitors

Miniature disc ceramic

100pF	1	YC2
270pF	1	YC1
10nF	3	YC3, 6, 7
47nF	1	YC4

Electrolytic 16V, radial

1 μ F	3	YCB, 10, 12
10 μ F	1	YCB
22 μ F	2	YCB, 11
100 μ F	1	YC13

Semiconductors

Diodes

1N4148	2	YD1, 2
--------	---	--------

Transistors

BC109	4	YTr1-4
-------	---	--------



Integrated Circuits

TA7130	1	YIC1
--------	---	------

Miscellaneous

Printed circuit board; i.f. transformer
YRCS11098AC; miniature coaxial cable.

WRM243

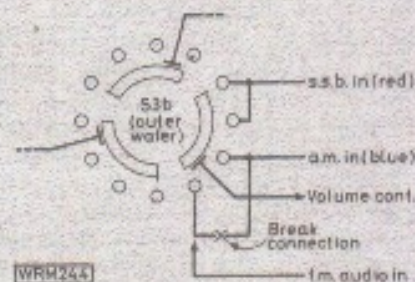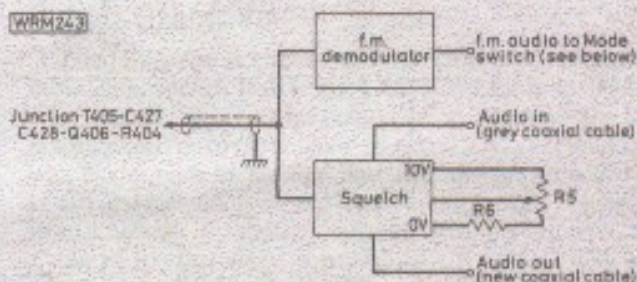

WRM244

Fig. 3.3: Connection details for the new board to the FRG-7

peaked and the easiest way to do this is to find an f.m. transmission and trim it for the loudest and clearest audio output. In most areas a good source of f.m. transmissions is the UK CB service. Find a relatively weak signal and adjust Y1 for the best signal to noise ratio. Do not be surprised if some of the signals sound distorted, in the author's experience many CBers use badly adjusted accessories such as power microphones and echo boxes. However, if distortion is a persistent problem then refer to the section dealing with resistor R_y.

If all is well with the f.m. stage now test the squelch. There should be a definite switch-off point with no signal and it should be found that with the squelch set to just off, even a signal that does not register on the S-meter should open the squelch "gate". If problems are encountered, check with a voltmeter that there is a definite voltage